

## Circuit Elements &amp; Phasor Analysis

Circuit elements

Resistor

$$V \oplus \quad I \oplus \quad R \text{ } \left[ \right] \quad C \text{ } \left[ \right] \quad L \text{ } \left[ \right]$$

$$N = Ri \rightarrow p = N = Ri^2$$

Inductor


$$N = L \frac{di}{dt} \rightarrow p = Ni = Li \frac{di}{dt}$$

Capacitor

$$i = C \frac{dv}{dt} \rightarrow p = Ni = Cv \frac{dv}{dt}$$

Phasor Analysis & Sinusoidal ResponseSinusoidal voltage

$$v = V_m \cos(\omega t + \phi)$$

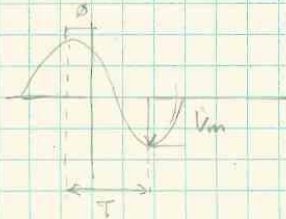

$$f = \frac{1}{T}$$

$$\omega = 2\pi f$$

$$\phi_{\text{deg}} = \frac{180^\circ}{\pi} \phi_{\text{rad}}$$

RMS Value

RMS current is the DC current that has the same average power dissipated through a resistor as current  $i(t)$  passes it

eg.  $p(t) = i^2(t)R$



$$P_{\text{avg}} = \frac{1}{T} \int p(t) dt = \frac{1}{T} \int i^2(t) R dt$$

not that rearranging:  $P_{avg} = \left[ \frac{1}{T} \int i^2 dt \right] R$

quantity inside is RMS value so

$$P_{avg} = (I_{rms})^2 R$$

Can calculate similarly for  $V$ . Note that

~~$P_{avg} = V_{rms} I_{rms}$~~  for sinusoids in phase

For sine wave:  $I_{rms} = \frac{I_m}{\sqrt{2}}$


$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \cos^2 \theta d\theta} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \frac{1 + \cos 2\theta}{2} d\theta}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \left[ \frac{\theta}{2} - \frac{\sin 2\theta}{2} \right]_0^{2\pi}}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \left( \frac{2\pi}{2} - \frac{\sin 2\pi}{2} \right) - \left( \frac{0}{2} - \frac{\sin 0}{2} \right)}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \cdot \frac{2\pi}{2}} = \frac{I_m}{\sqrt{2}} \checkmark$$

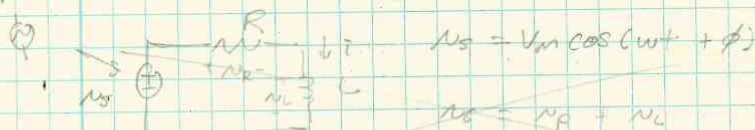Draw as Sinusoidal Response  $\rightarrow$



$$V_m \cos(\omega t + \phi) = Ri + L \frac{di}{dt} \quad \left. \vphantom{V_m \cos(\omega t + \phi)} \right\} \text{ differential equation}$$


PHASORSEuler's Identity

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$e^{-j\theta} = \cos\theta - j\sin\theta$$

$$\cos\theta = \operatorname{Re} e^{j\theta}$$
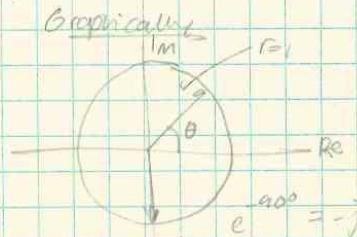
$$\sin\theta = \operatorname{Im} e^{j\theta}$$



$$v = v_m \cos(\omega t + \phi)$$

$$= v_m \operatorname{Re} e^{j(\omega t + \phi)}$$

$$= v_m \operatorname{Re} e^{j\omega t} e^{j\phi}$$

$$= \operatorname{Re} \{ v_m e^{j\phi} e^{j\omega t} \} = \vec{v} = v_m e^{j\phi} = \operatorname{Re} \{ v_m \cos(\omega t + \phi) \}$$

phasor = v\_m \angle \phi

Circuit Elements in Phasor DomainResistor

$$* \theta_i = -\theta$$

$$v = R i_m \cos(\omega t + \theta_i)$$

$$= R i_m \cos(\omega t + \theta_i)$$

$$\Rightarrow \vec{v} = R i_m e^{j\theta_i} = R i_m \angle \theta_i$$

$$\Rightarrow \vec{v} = R \vec{i}$$

Inductor

$$v = L \frac{di}{dt} = L \frac{d}{dt} (i_m \cos(\omega t + \theta_i))$$

$$= -\omega L i_m \sin(\omega t + \theta_i)$$

$$\Rightarrow v = -\omega L i_m \cos(\omega t + \theta_i - 90^\circ)$$

$$\vec{v} = -\omega L i_m e^{j\theta_i} e^{-j90^\circ}$$

$$\vec{v} = j\omega L i_m e^{j\theta_i} = j\omega L \vec{i}$$



Capacitor

$$i = C \frac{dv}{dt} = C \frac{d}{dt} [V_m \cos(\omega t + \phi_v)]$$


$$\vec{i} = j\omega C \vec{v}$$

$$\Rightarrow \vec{v} = \frac{1}{j\omega C} \vec{i}$$

Impedance

$$\vec{v} = \vec{z} \vec{i}$$

What is circuit?

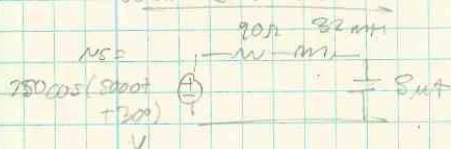

$$\vec{z}_L = j\omega L = j(5000)(82 \cdot 10^{-6}) = j160 \Omega$$

$$\vec{z}_C = j \frac{-1}{\omega C} = \frac{-j}{(5000)(82 \cdot 10^{-6})} = -j144 \Omega$$

$$\vec{v}_s = 750 \angle 30^\circ \text{ V}$$

$$\vec{z}_{in} = 90 + j160 - j144 = 90 + j16 \Omega$$

$$|z_{in}| = 90 \angle 10^\circ = 150$$

$$\vec{i} = \frac{\vec{v}_s}{\vec{z}_{in}} = \frac{750 \angle 30^\circ}{150 \angle 10^\circ} = 5 \angle 20^\circ \text{ A}$$

$$\theta_{in} = \tan^{-1}\left(\frac{16}{90}\right) = 10^\circ$$

$$= 5 \angle 20^\circ \text{ A}$$